



MICHIGAN ENGINEERING
UNIVERSITY OF MICHIGAN



**POWER ELECTRONICS AND
ENERGY RESEARCH STUDIOS**

EECS215 Discussion

240912

GSI: Inhwi Hwang

Covered area: Lectures in 08/26-09/09

Date: 240912 (05:30 pm – 06:30 pm)

Tips

- Understanding electrical circuits is fundamental to the study of electrical engineering, so it is beneficial to have a solid grasp of the basics.
- To ensure comprehension and achieve good grades, start by solving simple examples. Gradually tackle more challenging problems and contemplate them to develop a physical intuition.
- Ref: <https://ocw.mit.edu/courses/6-002-circuits-and-electronics-spring-2007/download/>, EECS215 lecture notes, and so on...
- Need some materials to recommend? (Problem sets, ...)


inhwi@umich.edu

Review

- KCL
- KVL
- Ohm's Law
- Equivalent circuit
- Source transformation

Review - KCL

$$I_1 + I_2 + I_3 = 0$$

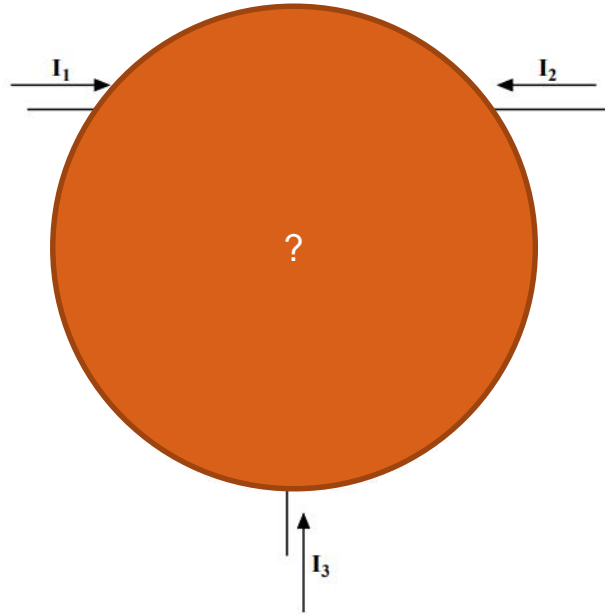

Review - KVL


Sum of voltages around a closed path is zero

Sum of voltage drops = sum of voltage rises

Result of Conservation of Energy Assumption

$$\sum_n V_n = 0$$

Define V_n 's +/- in direction of loop

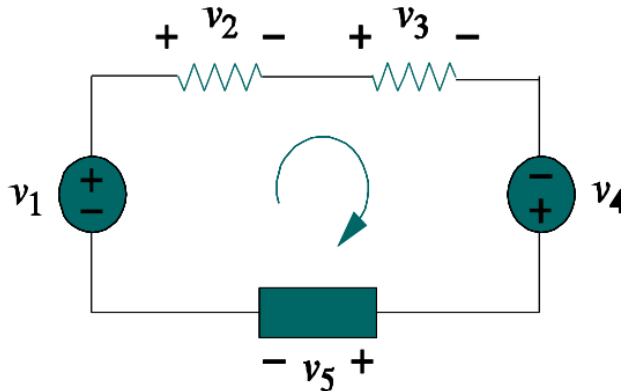

$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$


$$v_2 + v_3 + v_5 = v_1 + v_4$$

Review – Ohm's law


Voltage across resistor is proportional to current

$$v = iR$$

$$R = \frac{v}{i}$$

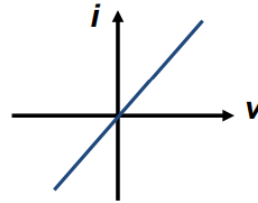

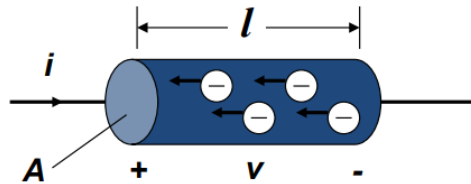Resistance: ability to resist flow of electric current




$$R = \frac{\rho l}{A} \text{ Standard units } \Omega$$

$$\rho = \text{Resistivity Standard units } \Omega - m$$

resistivity is a material parameter
(this should become clear in
230&320)

Review – Equivalent circuit

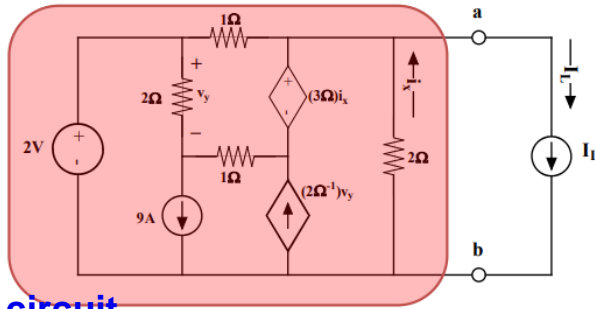If the circuit is **linear circuit**,
We can express this circuit
with following **two forms** at the two terminals




Only for **linear circuit**
(No matter dependent/independent sources)

- The i-v behavior at the output terminals (a,b) is the same even though the 3 circuit are different internally


Constant Voltage source
+

Series resistor
(Thevin equivalent)

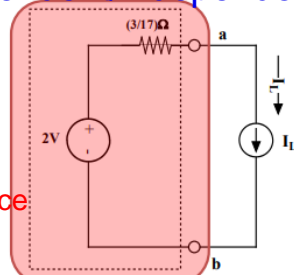

$$V_{ab} = R i_L + V_{oc}$$

$$y = ax + b$$

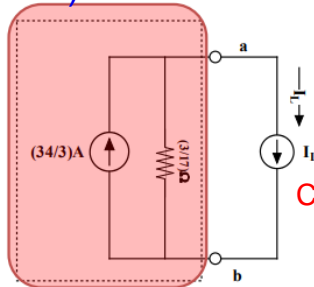



$$V_{ab} = R i_L + R i_{sc}$$

$$y = ax + b$$

Constant Current source
+
Paralleled resistor
(Norton equivalent)

Review – Source transformation

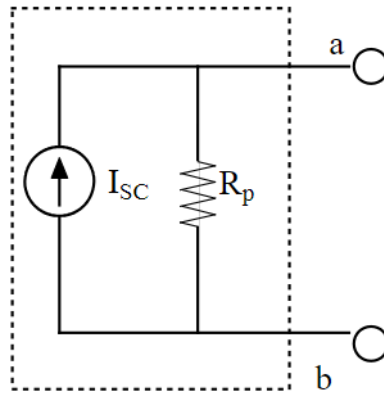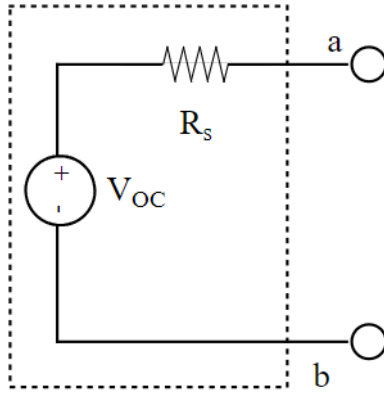- Viewed from the output terminals a&b, the two circuits below are *equivalent*
- Replacement of a circuit by an equivalent can make some problems easier to solve



$$R_S = R_P$$

$$V_{OC} = R_P I_{SC}$$

$$I_{SC} = V_{OC} / R_S$$

Problem set 0

$$(1) \quad t = \left[0 \text{ ms}, \frac{1}{240} \text{ ms} \right]$$

$$i(t) = 25 \sin(60\pi t) \text{ A}$$

Transferred charges: $\Delta q(t)$?

$$i(t) = 400 \text{ mA}$$

$$(2) \quad v(t) = 400 \text{ V}$$


$$p(t) = i(t)v(t)?$$

Supplied Power by X, $p_1(t)$?

Supplied Power to X, $p_2(t)$?


Supplied Power by Y, $p_3(t)$?

Supplied Power to Y, $p_4(t)$?

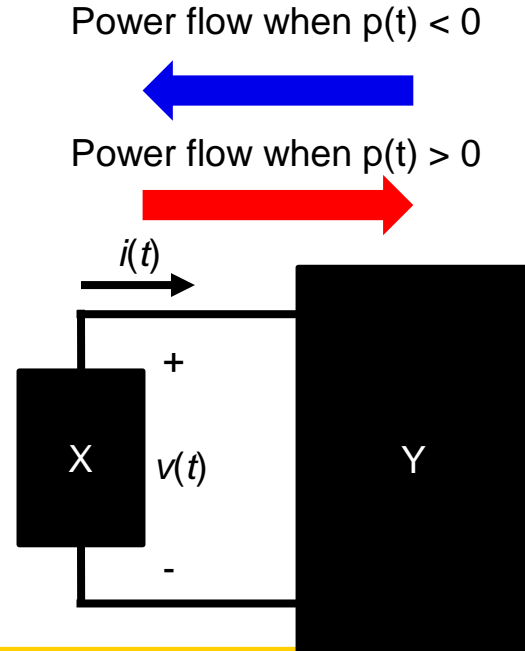

Problem set 1

$$V_o/V_s?$$

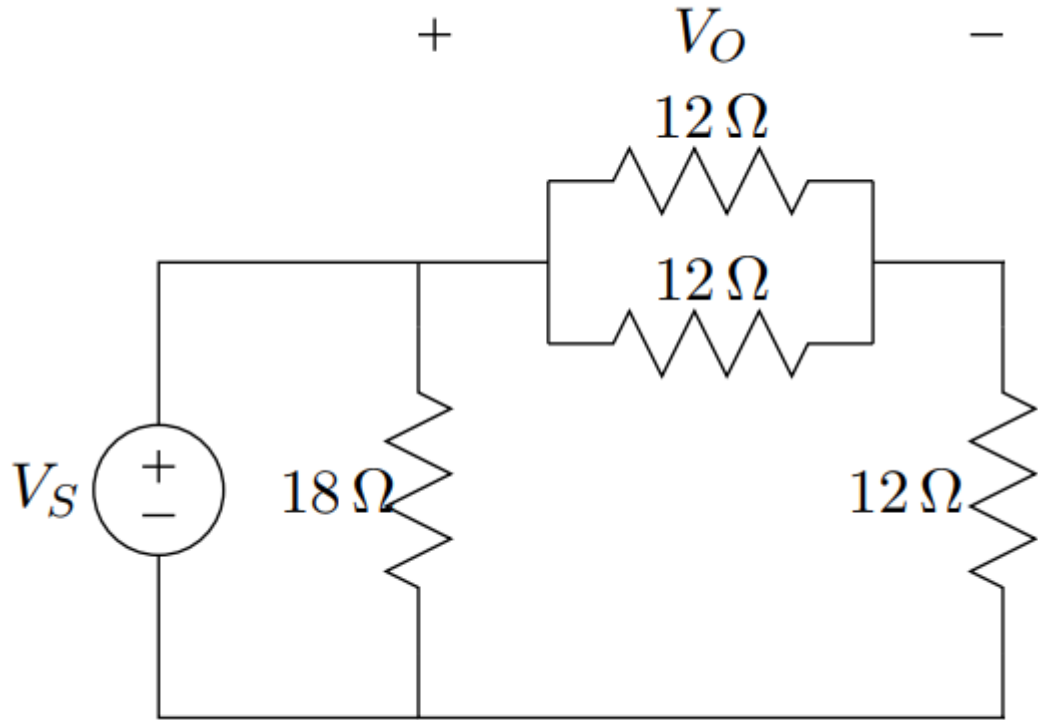

Problem set 2

The following two resistor circuit is assembled in a series connection, as one resistor follows the other in a series. For this circuit, answer the following questions.


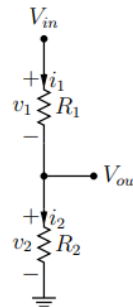


Figure 7: Circuit for problem 1. i_1 is the current flowing into R_1 and i_2 is the current flowing into R_2 . V_{out} is unconnected.


-
- What is the relationship between i_1 and i_2 ?
 - What is the voltage drop across R_1 in terms of i_1 and R_1 ?
 - What is the voltage drop across R_2 in terms of i_2 and R_2 ?
 - What is the voltage at V_{out} in terms of v_2 ?
 - What is the voltage at V_{in} in terms of v_2 and v_1 ?
 - What is the relationship between V_{in} and V_{out} in terms of R_1 and R_2 ? (Note that this is the voltage divider equation)
 - What is V_{in}/i_1 in terms of R_1 , and R_2 ? (Note that this is the formula for summing resistors in series)

Problem set 3

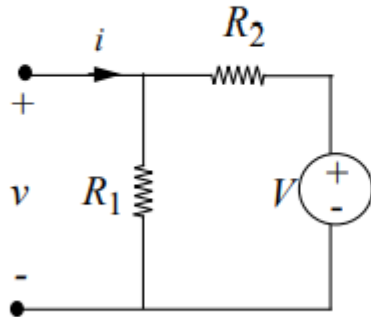Problem 2.1: Find the Thevenin and Norton equivalents of the following networks, and graph their i - v relations as viewed from their ports. (*Hint: use superposition for Network B.*)



Network (A)


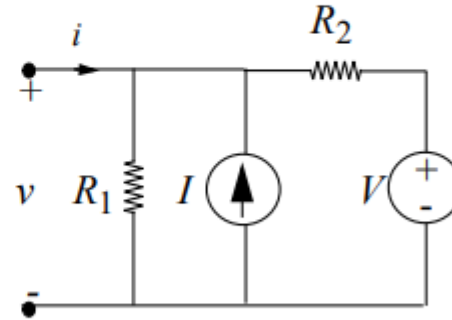


Network (B)


Problem set 4

Problem 2.3: Two networks, N1 and N2, are described graphically in terms of their i - v relations, and connected together through a single resistor, as shown below.

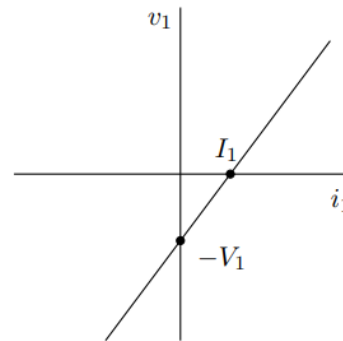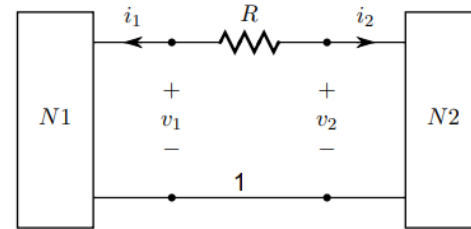- (A) Find the Thevenin and Norton equivalents of N1 and N2.
- (B) Find the voltages v_1 and v_2 that result from the interconnection of N1 and N2.



(a) Network 1 (N1)

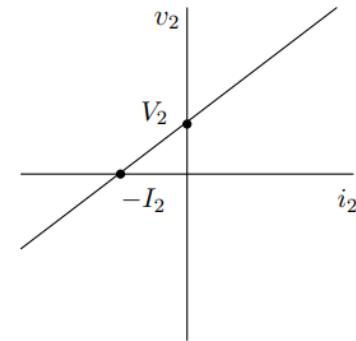

(b) Network 2 (N2)